



National University of Sciences and Technology (NUST)

School of Electrical Engineering and Computer Science

EE-421 Digital System Design

Instructor: Dr Rehan Ahmed

Assignment: 2

Due Date: 22nd May 2022

Total Marks: 100

Submitted By :

Name	ID
Ch. Muhammad Shaheer Yasir	286021
Muhammad Hamza	290951

NuCORE Module:

```
module NuCore (KEY, SW, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, instruction, current_pc, Zero);

input [0:0] KEY;

input [0:0] SW;

output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;

wire clock, reset;

input [38:0] instruction;

output Zero;

wire [63:0] ALUOut;

output reg [5:0] current_pc;

wire [3:0] Address_A, Address_B;

wire [31:0] Write_Data_A, Write_Data_B;

wire [31:0] Read_Data_A, Read_Data_B;

wire [2:0] opcode;


assign clock = KEY[0];

assign reset = SW[0];


always @(posedge clock)

begin
if (reset)
current_pc <= 0;
else
current_pc <= current_pc + 1;
end


//instructionMemory U0 (reset, current_pc, instruction);

assign opcode = instruction [38:36];

decode U1 (clock, instruction, Address_A, Address_B, Write_Data_A, Write_Data_B);
```

```

reg_A U2 (clock, opcode, reset, Address_A, Write_Data_A, Read_Data_A);
reg_B U3 (clock, opcode, reset, Address_B, Write_Data_B, Read_Data_B);
ALU U4 (clock, opcode, Read_Data_A, Read_Data_B, ALUOut, Zero);
display U5(ALUOut[3:0], HEX0);
display U6(ALUOut[7:4], HEX1);
display U7(Read_Data_A[3:0], HEX2);
display U8(Read_Data_A[7:4], HEX3);
display U9(Read_Data_B[3:0], HEX4);
display U10(Read_Data_B[7:4], HEX5);
endmodule

module decode (clock, instruction, Address_A, Address_B, Write_Data_A, Write_Data_B);
input [38:0] instruction;
input clock;
output reg [3:0] Address_A, Address_B;
output reg [31:0] Write_Data_A, Write_Data_B;
wire [2:0] opcode;
assign opcode = instruction [38:36];

always @(*)
begin
if (opcode == 3'b001)
begin
Address_A = instruction[35:32];
Write_Data_A = instruction[31:0];
end
else if (opcode == 3'b010)
begin
Address_B = instruction[35:32];
Write_Data_B = instruction[31:0];
end
else if (opcode == 3'b011 | opcode == 3'b100 | opcode == 3'b101 | opcode == 3'b110 | opcode == 3'b111)

```

```

begin
    Address_A = instruction[35:32];
    Address_B = instruction[31:28];
end

end

endmodule

module reg_A (clock, opcode, reset, Address_A, Write_Data_A, Read_Data_A);
input [2:0] opcode;
input [3:0] Address_A;
input [31:0] Write_Data_A;
input reset, clock;
output reg [31:0] Read_Data_A;
integer k;

reg [31:0] reg_file_A [15:0];
always @(*)
begin
    if (reset)
    begin
        for (k = 0; k < 16; k = k + 1);
        begin
            reg_file_A[k] <= 32'b0;
        end
    end
    else if (opcode == 3'b001)
    begin
        reg_file_A[Address_A] <= Write_Data_A;
    end
    else if (opcode == 3'b011 | opcode == 3'b100 | opcode == 3'b101 | opcode == 3'b110 | opcode == 3'b111)

```

```

        begin
            Read_Data_A <= reg_file_A[Address_A];
        end
    end
end

```

```

endmodule

```

```

module reg_B (clock, opcode, reset, Address_B, Write_Data_B, Read_Data_B);

```

```

    input [2:0] opcode;

```

```

    input [3:0] Address_B;

```

```

    input [31:0] Write_Data_B;

```

```

    input reset, clock;

```

```

    output reg [31:0] Read_Data_B;

```

```

    integer k;

```

```

    reg [31:0] reg_file_B [15:0];

```

```

    always @(*)

```

```

    begin

```

```

        if (reset)

```

```

        begin

```

```

            for (k = 0; k < 16; k = k + 1);

```

```

            begin

```

```

                reg_file_B[k] <= 32'b0;

```

```

            end

```

```

        end

```

```

        else if (opcode == 3'b010)

```

```

        begin

```

```

            reg_file_B[Address_B] <= Write_Data_B;

```

```

        end

```

```

        else if (opcode == 3'b011 | opcode == 3'b100 | opcode == 3'b101 | opcode == 3'b110 | opcode == 3'b111)

```

```

        begin

```

```

        Read_Data_B <= reg_file_B[Address_B];

    end

end

endmodule

module ALU (clock, opcode, Read_Data_A, Read_Data_B, ALUOut, Zero);
input [2:0] opcode;
input [31:0] Read_Data_A, Read_Data_B;
input clock;
output reg [63:0] ALUOut;
output reg Zero;

always @(*)
begin
case(opcode)
3'b000: ALUOut = 63'd0;

3'b011: ALUOut = Read_Data_A + Read_Data_B;

3'b100: ALUOut = Read_Data_A - Read_Data_B;

3'b101: ALUOut = Read_Data_A | Read_Data_B;

3'b110: ALUOut = Read_Data_A & Read_Data_B;

3'b111: ALUOut = Read_Data_A << Read_Data_B;

default: ALUOut = 63'd0;

endcase

```

```
Zero = (ALUOut == 63'd0);
```

```
end
```

```
endmodule
```

```
module display (A, Disp);
```

```
input [3:0] A;
```

```
output reg [6:0] Disp;
```

```
always @(*) begin
```

```
case (A)
```

```
4'd0 : Disp = 7'b1000000;
```

```
4'd1 : Disp = 7'b1111001;
```

```
4'd2 : Disp = 7'b0100100;
```

```
4'd3 : Disp = 7'b0110000;
```

```
4'd4 : Disp = 7'b0011001;
```

```
4'd5 : Disp = 7'b0010010;
```

```
4'd6 : Disp = 7'b0000010;
```

```
4'd7 : Disp = 7'b1111000;
```

```
4'd8 : Disp = 7'b0000000;
```

```
4'd9 : Disp = 7'b0010000;
```

```
4'd10 : Disp = 7'b0001000;
```

```
4'd11 : Disp = 7'b0000011;
```

```
4'd12 : Disp = 7'b1000110;
```

```
4'd13 : Disp = 7'b0100001;
```

```
4'd14 : Disp = 7'b0000110;
```

```
4'd15 : Disp = 7'b0001110;
```

```
endcase
```

```
end
```

```
endmodule
```

Instruction Memory Module:

[illegible]


```
end
endmodule
```

Test bench module :

```
module testbench;
```

```
reg [0:0] KEY;
```

```
reg [0:0] SW;
```

```
wire [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
```

```
reg [38:0] instruction;
```



```
wire [5:0] current_pc;
```

```
NuCore DUT(KEY[0], SW[0], HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, instruction, current_pc);
```


```
instructionMemory DUT1 (SW[0], current_pc, instruction);
```

```
endmodule
```


Test Bench Simulation Waveform:

  

FPGAs OUTPUTS:

 



 

BLOCK LEVEL DIAGRAM:

